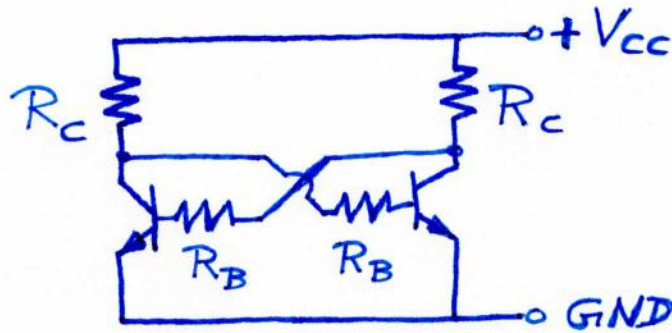


ITE - Homework 11 - Solution

Problem 1 SRAM cell


(a) BJT SRAM cell



One of the two branches is ON \Rightarrow Current flowing. One BJT is in saturation (ON or conductive) and a voltage drops across R_c .

The approximate power consumption is given by $P = \frac{V_{cc}^2}{R_c}$

(b) CMOS FET SRAM cell

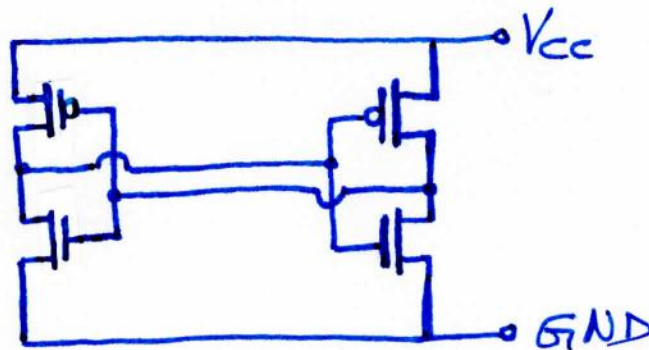

None of the two branches is fully ^② conductive. In each branch, one of the FETs is always OFF. \Rightarrow
 $I = 0$ in each branch. $\Rightarrow P = 0$


(c) BJT SRAM is not suitable for high degrees of integration because the power consumption is too high \Rightarrow Heat problem.

Problem 2


CMOS inverter

3

(a) Circuit diagram

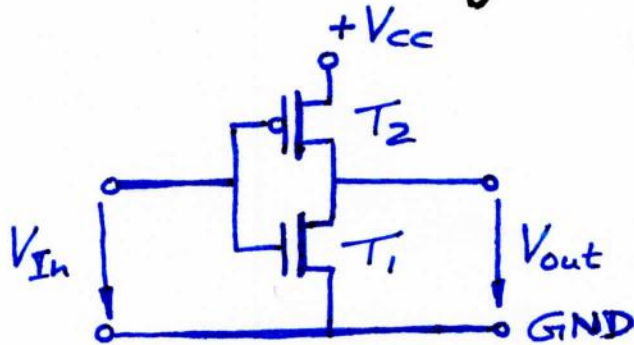

Alternative circuit diagram

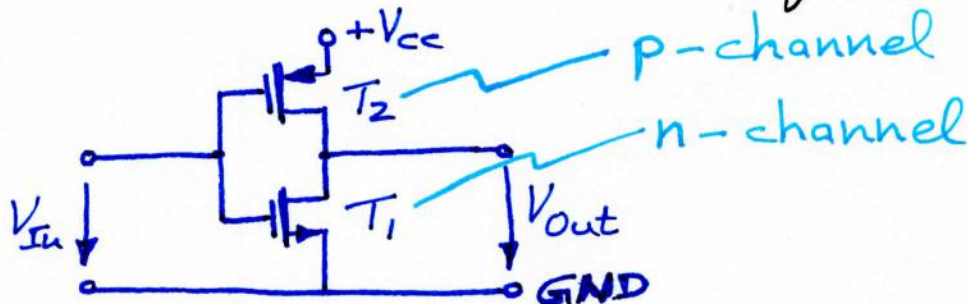

T_1 turns ON for $+V_{GS}$

T_2 turns ON for $-V_{GS}$

V_{In} is either $+V_{cc}$ or GND

$$V_{In} = +V_{cc} \Rightarrow T_1 = \text{ON} \quad T_2 = \text{OFF}$$

$$\Rightarrow V_{out} = 0$$

$$V_{In} = \text{GND} \Rightarrow T_1 = \text{OFF} \quad T_2 = \text{ON}$$

$\rightarrow 0V$

$$\Rightarrow V_{out} = +V_{cc}$$

(b) Small-signal equivalent circuit is of no interest because we have no small-signal source.


- (c) Static power consumption is always zero, because one of the FETs is always OFF.
- (d) Power consumption of CMOS FET inverter is zero \Rightarrow No heat problem.
- (e) Power consumption of BJT inverter is always > 0 (greater zero).
BJT has finite input impedance ($< \infty$) \Rightarrow Big heat problem.

Problem 3

CMOS inverter

(a) LHS circuit has resistive load


T_1 output characteristic

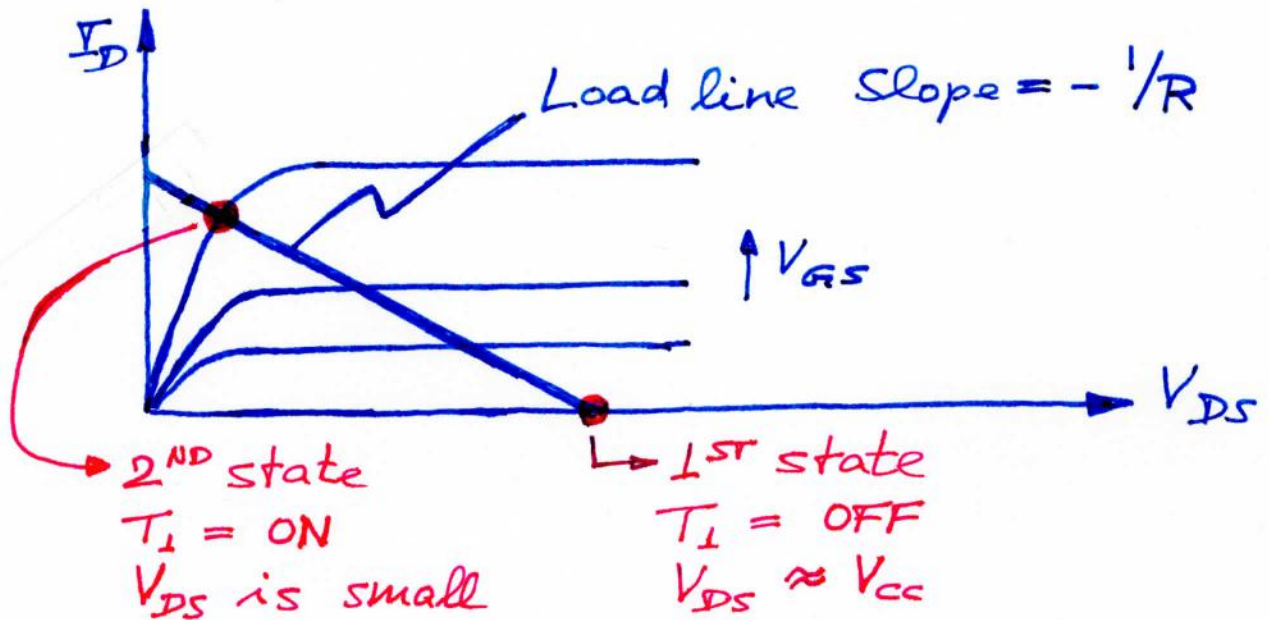

1ST state $\Rightarrow I_D = 0$

2ND state $\Rightarrow I_D \neq 0$

(b) RHS circuit has T_2 as load

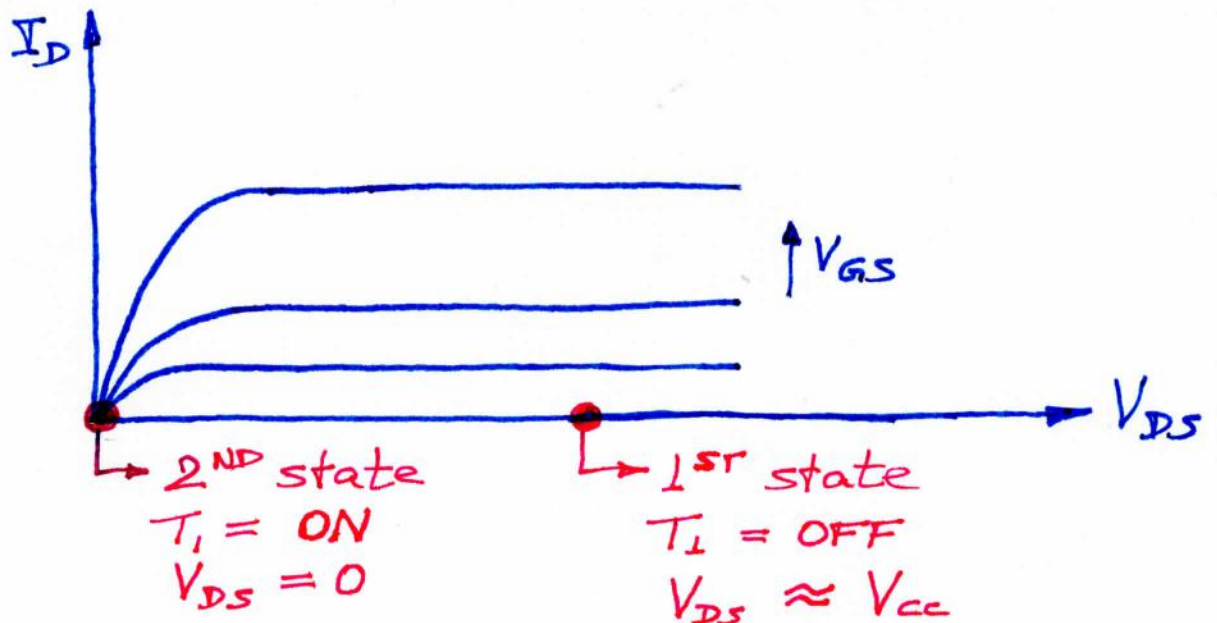

Note that $I_D = 0$ in 1st and 2nd state ⑥
state \Rightarrow No power consumption

(c) LHS circuit consumes power
 $P = V_{cc}^2 / R$. Power consumption is
not good for VLSI (very large scale
integration). \Rightarrow Heat problem.

RHS circuit, a CMOS circuit,
consumes no power \Rightarrow **No** heat
problem \Rightarrow Suitable for VLSI.

Problem 4

True/false statements

⑦

- (a) True Heat problem of BJTs prevents them from being used in VLSI (very large scale integrated circuits).
- (b) True The $Z_{in} = \infty$ characteristic of FETs makes them very suitable for the amplification of weak signals.