

# Small signal versus Large signal

## Linear systems:

Output  $\propto$  Input

Current  $\propto$  Voltage

Effect  $\propto$  Cause

Mathematics:  $y = cx \Rightarrow y \propto x$

$$F(ax) = aF(x)$$

## Non-linear systems

Effect not  $\propto$  Cause

## Linear circuit elements

R   $\Rightarrow I \propto V$

C   $\Rightarrow I \propto V$

L   $\Rightarrow I \propto V$


## Non-linear circuit elements

Diode   $\Rightarrow I \propto \exp(V)$

BJT   $\Rightarrow I_c \propto \exp(V_{BE})$


FET   $\Rightarrow I_D \propto g_m(V - V_{th})$

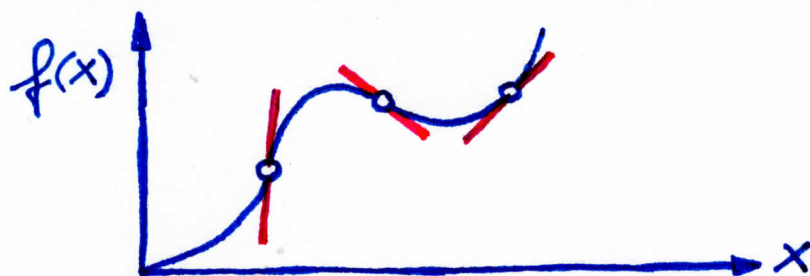Mathematics: Any non-linear function  $f(x)$  can be linearized in the vicinity of a point  $x$ .



Electronics: Any non-linear circuit can be linearized in the vicinity of its operating point.


Example: Diode

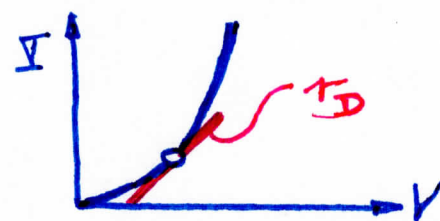

$$r_D = \frac{dV}{dI} = \left( \frac{dI}{dV} \right)^{-1}$$

⇒ For small signals, near a certain operating point, the diode has the differential resistance  $r_D = \frac{dV}{dI} \Big|_{\text{operating point}} = \left( \frac{dI}{dV} \right)^{-1} \Big|_{\text{oper. point}}$

# Small-signal input impedance of BJT ③

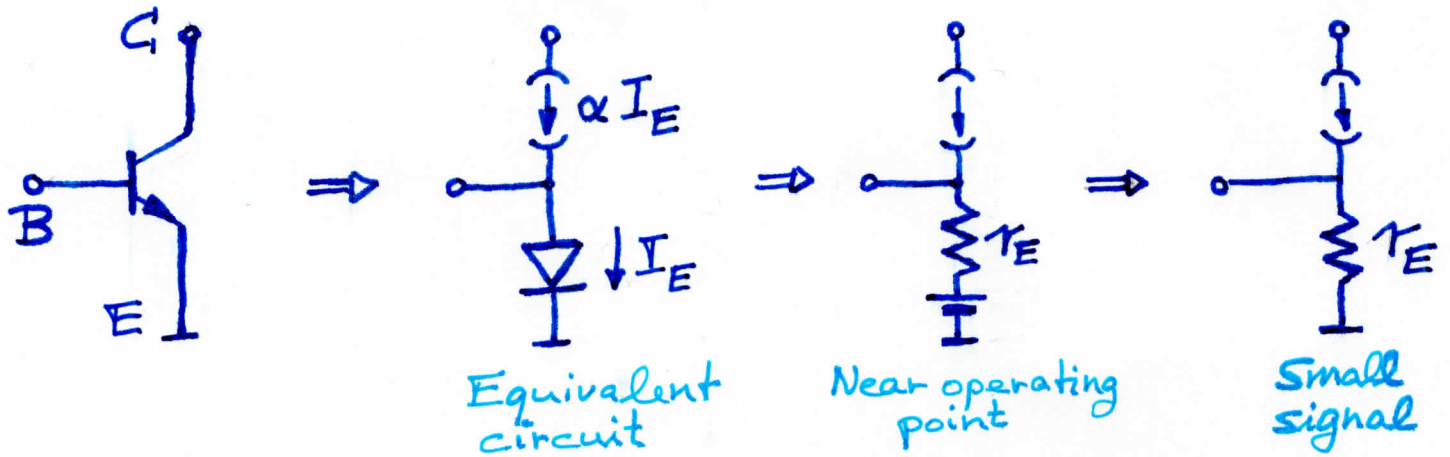

Small-signal  $r_E$  resistance (input resistance)  
 $\hookrightarrow$  emitter

$$\begin{aligned}
 r_E &= \frac{dV}{dI} = \left( \frac{dI}{dV} \right)^{-1} = \left( \frac{dI_E}{dV_{BE}} \right)^{-1} = \left( \frac{d}{dV_{BE}} I_E \right)^{-1} \\
 &= \left( \frac{d}{dV_{BE}} I_0 (e^{V_{BE}/V_t} - 1) \right)^{-1} \approx \left( \frac{d}{dV_{BE}} I_0 e^{V_{BE}/V_t} \right)^{-1} \\
 &= \left( I_0 e^{V_{BE}/V_t} \frac{1}{V_t} \right)^{-1} = \left( \frac{I_E}{V_t} \right)^{-1} = \frac{V_t}{I_E}
 \end{aligned}$$

$$\Rightarrow \boxed{r_E = \frac{V_t}{I_E}}$$

Also  $r_E = \frac{V_t}{I_E} = \frac{V_t}{I_B (\beta + 1)} \approx \frac{V_t}{\beta I_B}$