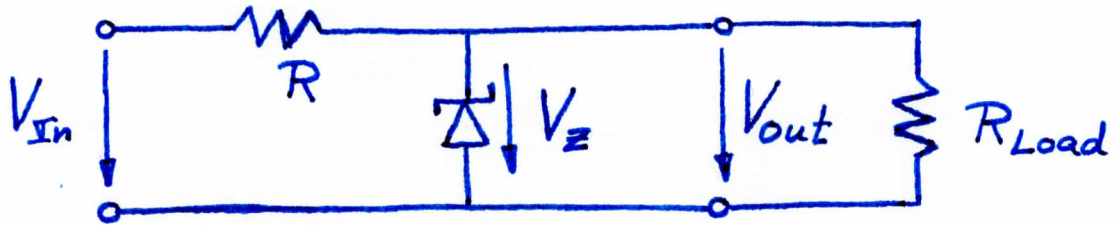


Zener diode applications

Voltage stabilization






$$\Rightarrow V_{out} = V_Z = \text{constant}$$

\Rightarrow Circuit consumes power even if $R_{Load} = \infty$

$\Rightarrow R_{Load}$ cannot be arbitrarily small. For example, if $R_{Load} = 0$, then $V_{out} = 0$.





Voltage clipper

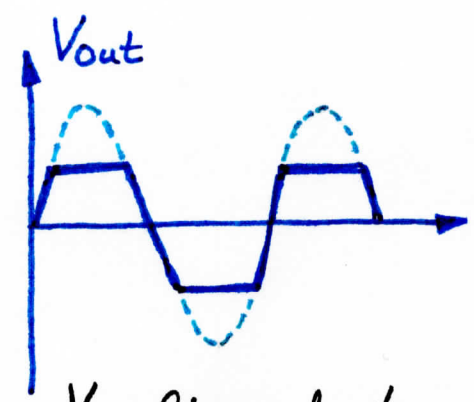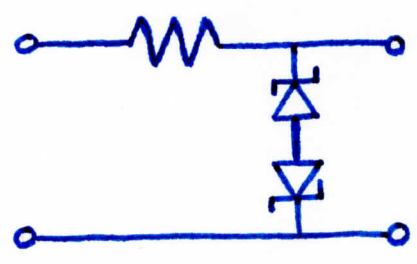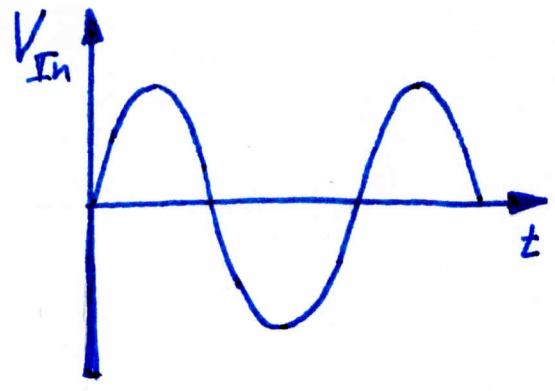


V clipped at $V_Z + V_{th} = V_Z + 0.7V$

Input voltage must be greater than V_Z .



How about the following circuits ?

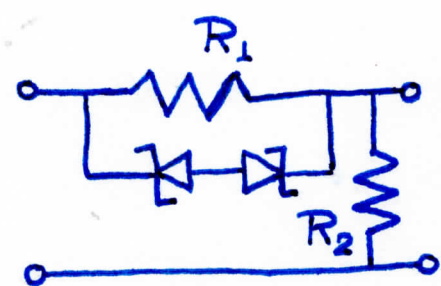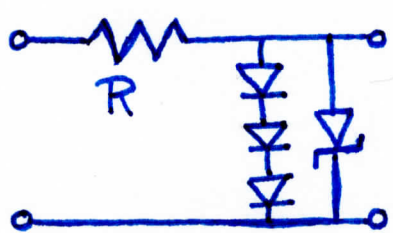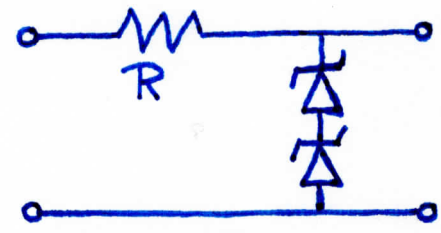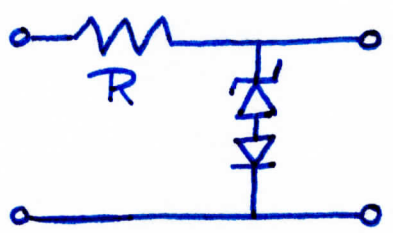

Voltage shifter

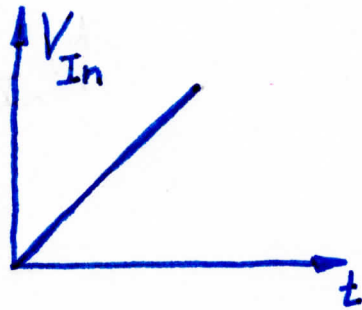

$$V_{In} = \alpha t$$

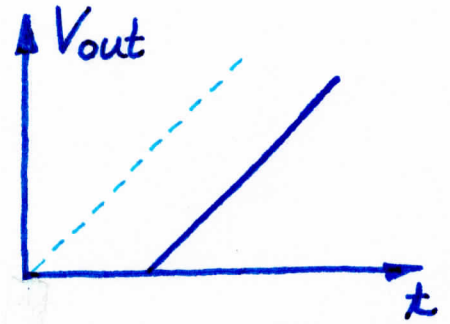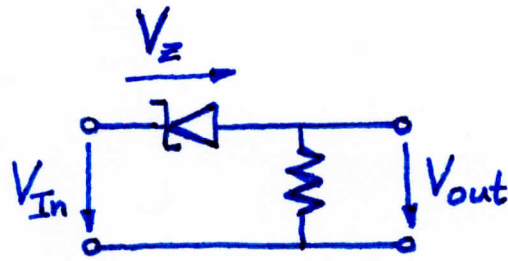

$$V_{out} = \alpha t - V_Z$$