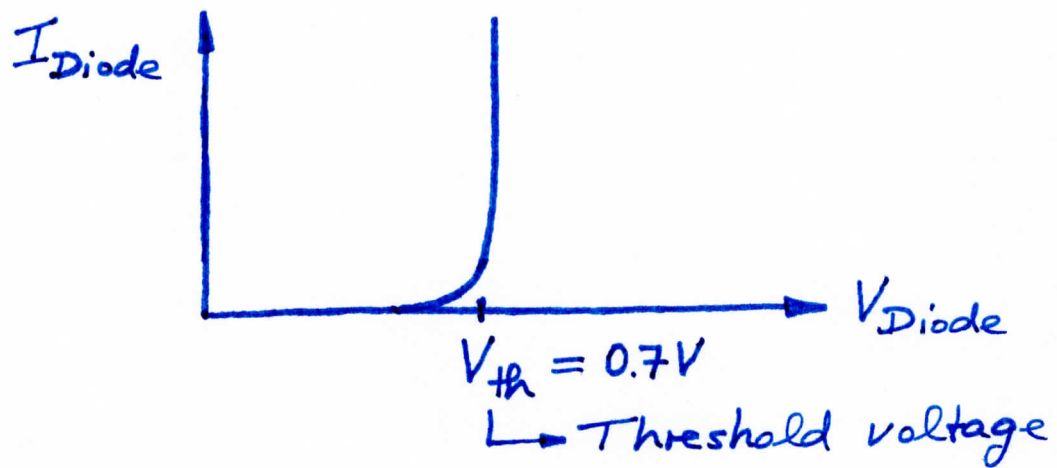


①

Small signal equivalent circuit of diode

Recall: $I = I_0 (e^{V/V_t} - 1)$
 $\approx I_0 e^{V/V_t}$ (forward bias)
 ... Shockley diode equation




Recall: $r_{Diode} = r_D = \frac{V_t}{I_{Diode}}$

Thermal voltage 26 mV

DC operating point (Quiescent point) (Q-point)

②


Linearization of IV characteristic

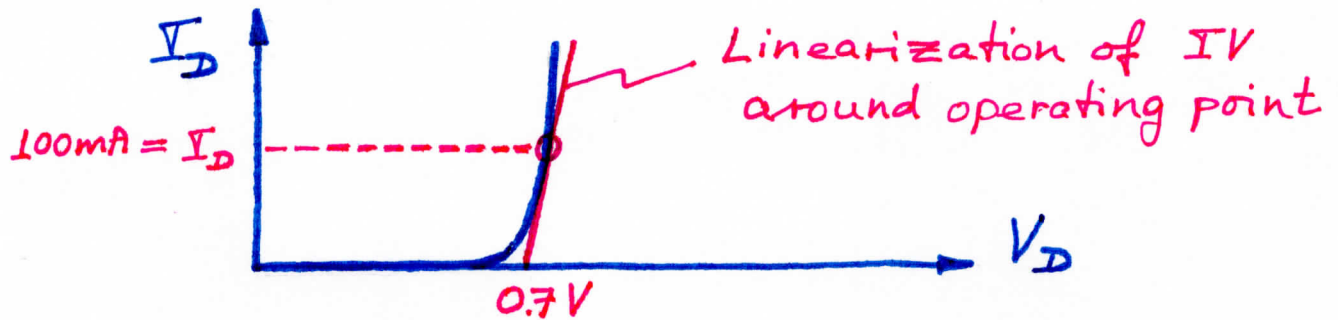


$$\Rightarrow r_D = \frac{V_T}{I_D} = \frac{26\text{mV}}{100\text{mA}} = \underline{\underline{0.26\Omega}}$$

Low resistance due to forward bias

Examples of linearization

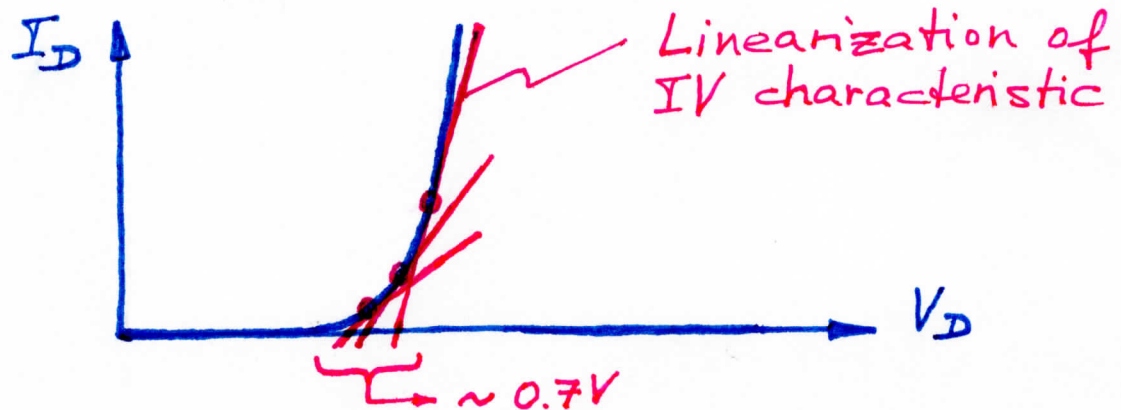

Equivalent circuit of linear IV line ?

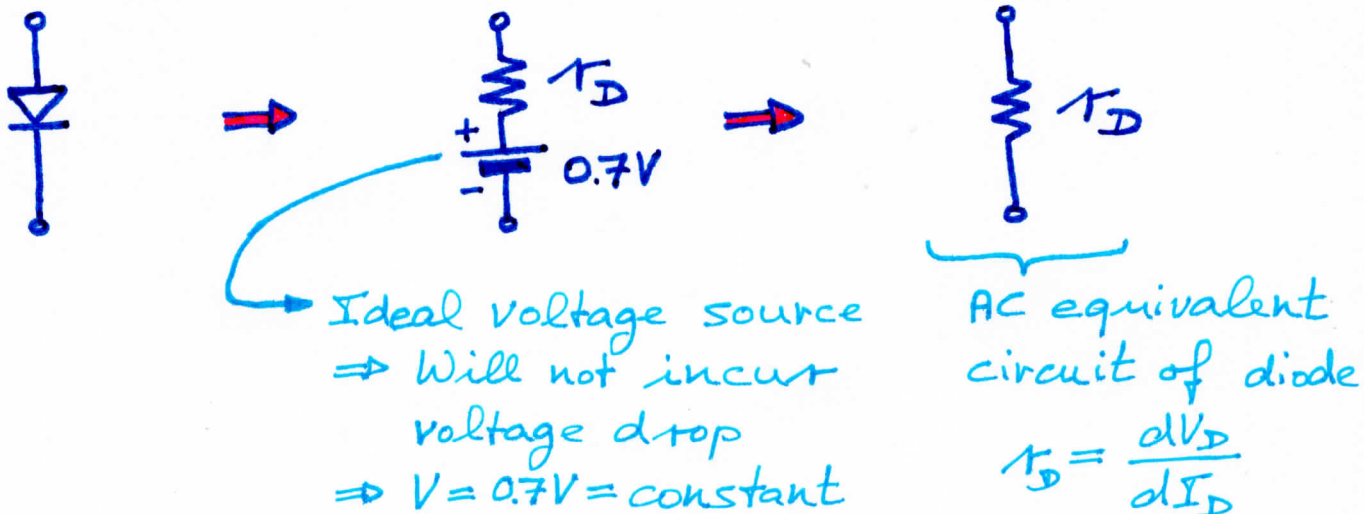


What is advantage of linearization? ③

⇒ We now have a linear circuit

⇒ We now can use the superposition theorem

Example

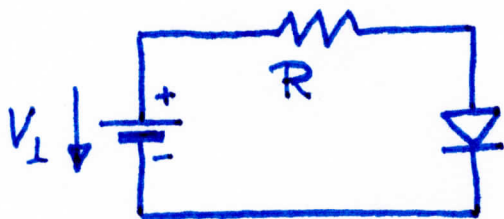

$$V_1 = 5V$$

$$R = 1k\Omega$$


Determine the DC operating point

⇒ KVL $V_1 = IR + V_{Diode}$

$$\Rightarrow I = \frac{V_1 - V_{Diode}}{R} = \frac{5V - 0.7V}{1k\Omega} = \frac{4.3V}{1k\Omega} = 4.3mA$$

$$\Rightarrow r_D = \frac{V_t}{I} = \frac{26mV}{4.3mA} = 6.05\Omega$$

Let us add a small AC signal

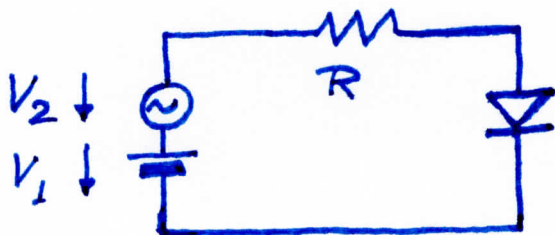


$$V_1 = 5V \text{ (DC)}$$

$$V_2 = 10mV \text{ (AC)}$$

$$R = 100\Omega$$

Linearization of circuit

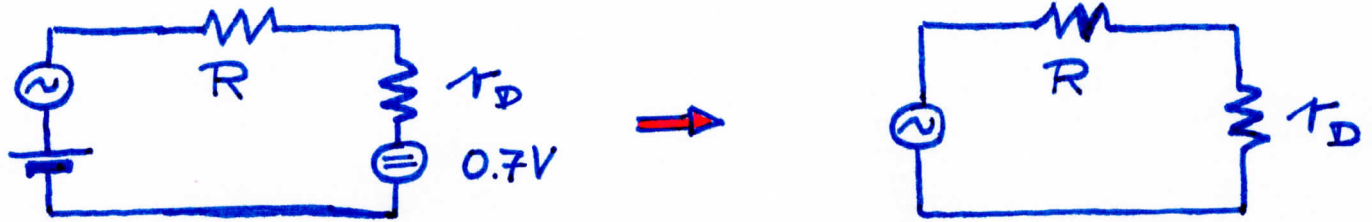

Superposition principle: We can separately consider the effect of each source

Also recall: Resistance of ideal voltage source is zero. \Rightarrow No additional voltage drop across sources.

$$\Rightarrow I_{DC} = \frac{5V - 0.7V}{100\Omega} = \frac{4.3V}{100\Omega} = 43 \text{ mA}$$

$$r_D = V_t / I = 26 \text{ mV} / 43 \text{ mA} = 0.6\Omega$$

\Rightarrow AC voltage drop across diode

$$\begin{aligned} V_{AC, \text{Diode}} &= \frac{r_D}{R + r_D} V_{AC} \quad (\text{Voltage divider}) \\ &= \frac{0.6\Omega}{100\Omega + 0.6\Omega} 10 \text{ mV} = \underline{\underline{0.06 \text{ mV}}} \end{aligned}$$

Summary: Train of thought

We have a non-linear circuit (e.g. diode circuit)



We wish to linearize the circuit (Why?)



We need to identify the point around which the circuit is linearized

(\Rightarrow DC operating point \Rightarrow Quiescent point \Rightarrow Q-point)



We determine the differential properties (e.g. differential resistance) of components (e.g. diode) at the Q-point

DC analysis



We can now calculate the effect of a small-signal AC input voltage (Why small signal? Why AC?)

AC analysis