

1) Laplace transforms/Transfer functions

Use Laplace transform tables!!!!

1.1: Find the Laplace transform of

$$f(t) = (\cos(2t) + e^{-4t}) \cdot u(t) \quad (\text{simplify into one ratio})$$

$$(s(s+4) + (s^2+4)) / ((s+4)(s^2+4))$$

$$(2s^2+4s+4) / (s^3+4s^2+4s+16)$$


1.2: Find the poles and zeros of the following functions. Indicate any repeated poles and complex conjugate poles. Expand the transforms using partial fraction expansion.

$$1. \quad F(s) = \frac{20}{(s+3)(s^2+8s+25)} \quad \begin{array}{l} \text{zeroes: None} \\ \text{poles: } -3, -4 \pm 3j \text{ (complex conjugates)} \end{array}$$


$$2. \quad F(s) = \frac{s^2+9s+6}{s^4+9s^3+34s^2+90s+100} = A_1/(s+2) + A_2/(s+5) + A_3/(s+1-3j) + A_3^*/(s+1+3j)$$

zeroes: $-0.725, -8.27$
 $(x+2)(x+5)(x^2+2x+10)$ poles: $-2, -5, -1 \pm 3j$ (complex conjugates)

2) Circuits and Differential Equations

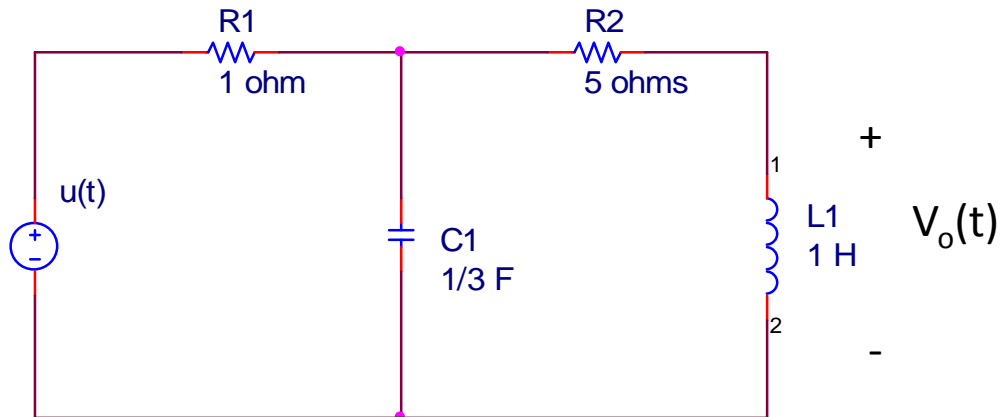

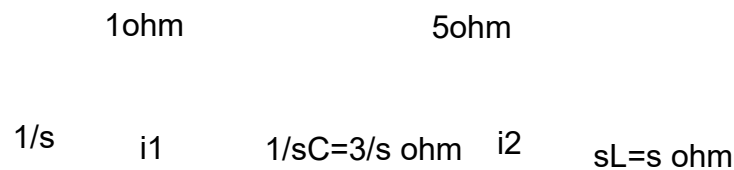2.1: Draw the s-domain equivalent circuit. Assume all initial conditions are zero and the source is an arbitrary source.



i_1 and i_2 ccw
positive is up and right, current flow is down and left

2.2 Using impedances, determine the expression for $V_o(t)$. Consider using mesh analysis then make one ratio.

$$\begin{aligned}
 -V(V_1) - V(R_1) + V(C) &= 0 \\
 1/s + i_1 + (i_1 - i_2) \cdot 3/s &= 0 \\
 1/s + i_1 + i_1 \cdot 3/s + i_2 \cdot -3/s &= 0 \\
 1/s + i_1(1 + 3/s) + i_2(-3/s) &= 0 \\
 i_1(1 + 3/s) + i_2(-3/s) &= -1/s \\
 i_2(1/3)(s^2 + 5s + 3)(1 + 3/s) + i_2(-3/s) &= -1/s \\
 i_2(s^2/3 + 5s/3 + 1 + s + 5 + 3/s - 3/s) &= -1/s \\
 i_2(s^2/3 + 8s/3 + 6) &= -1/s \\
 i_2 &= -1/(s(s^2/3 + 8s/3 + 6))
 \end{aligned}$$

$$\begin{aligned}
 -V(C) - V(R_2) + V(L) &= 0 \\
 -(i_1 - i_2) \cdot 3/s + i_2 \cdot 5 + i_2 \cdot s &= 0 \\
 -i_1 \cdot 3/s + i_2 \cdot 3/s + i_2 \cdot 5 + i_2 \cdot s &= 0 \\
 i_1(-3/s) + i_2(s + 5 + 3/s) &= 0 \\
 i_2(s + 5 + 3/s) &= i_1(3/s) \\
 i_2(1/3)(s^2 + 5s + 3) &= i_1
 \end{aligned}$$

$$\begin{aligned}
 V_0(s) &= s \cdot i_2 \\
 V_0(s) &= -1/(s^2/3 + 8s/3 + 6) \\
 V_0(s) &= -3/(s^2 + 8s + 18)
 \end{aligned}$$

2.3 Find $V_o(t)$ which is the $V_L(t)$ for $t > 0$ using $V_s = 1 u(t)$.

$$s^2 + 8s + 18 = 0$$

$$s = -4 \pm j\sqrt{2}$$

$$A_1/(s+4+j\sqrt{2}) + A_1^*/(s+4-j\sqrt{2}) = -3/((s+4-j\sqrt{2})(s+4+j\sqrt{2}))$$


$$A_1 = 3/(2j\sqrt{2})$$

$$A_1^* = -3/(2j\sqrt{2})$$

$$3/(2j\sqrt{2})/(s+4+j\sqrt{2}) - 3/(2j\sqrt{2})/(s+4-j\sqrt{2})$$

$$3/(2j\sqrt{2}) * e^{(-4-j\sqrt{2})t} - 3/(2j\sqrt{2}) * e^{(-4+j\sqrt{2})t}$$

3) RLC and initial conditions

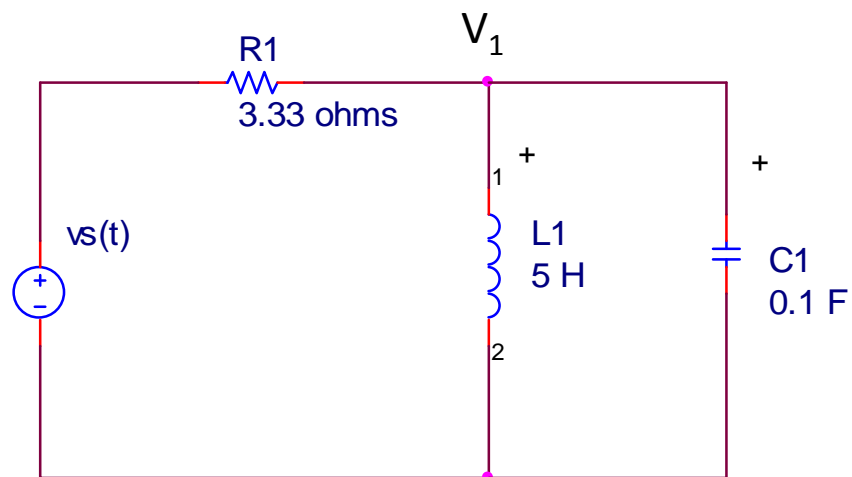

$$v_s(t) = 10u(t)$$

AND assume that -1A flows through the inductor and +5V is across the capacitor at $t=0$i.e. $v_c(0)=5$ and $i_L(0)=-1$

3.1: Draw the s-domain equivalent with initial conditions.

10/3 ohm

5s ohm

10/s ohm

+
10/s V
-


-
-5V
+ +
5V
-

+
5/s V
-

3.2: Find the value of the voltage across the capacitor, $v_c(t)$, using nodal analysis (at node V1) and laplace.

$$\begin{aligned}
 IR + IL + IC &= 0 \\
 VR/RR + VL/RL + VC/RC &= 0 \\
 (V1 - 10/s)/(10/3) + (V1 - 5)/(5s) + (V1 - 5/s)/(10/s) &= 0 \\
 (V1 - 10/s)(3/10) + (V1 - 5)(1/5s) + (V1 - 5/s)(s/10) &= 0 \\
 (3/10 * V1 - 3/s) + (1/5s * V1 - 1/s) + (s/10 * V1 - .5) &= 0 \\
 V1(3/10 + 1/5s + s/10) + (-3/s - 1/s - .5) &= 0 \\
 V1(s/10 + 3/10 + 1/5s) &= (.5 + 4/s) \\
 V1 &= (5s + 40)/(s^2 + 3s + 2) \\
 V1 &= 5 * (s + 8)/((s + 1)(s + 2)) \\
 V1/5 &= A/(s + 1) + B/(s + 2) \\
 A(s + 2) + B(s + 1) &= (s + 8) \\
 As + A2 + Bs + B &= s + 8 \\
 s(A + B) + (2A + B) &= s + 8 \\
 A + B &= 1, A = 1 - B, 2A + B = 8, 2(1 - B) + B = 8, 2 - B = 8, -6 = B, A = 7 \\
 V1/5 &= 7/(s + 1) - 6/(s + 2) \\
 V1 &= 35/(s + 1) - 30/(s + 2) \\
 V1(t) &= 35 * e^{-1*t} - 30 * e^{-2*t} * u(t)
 \end{aligned}$$

4) RLC parallel circuits

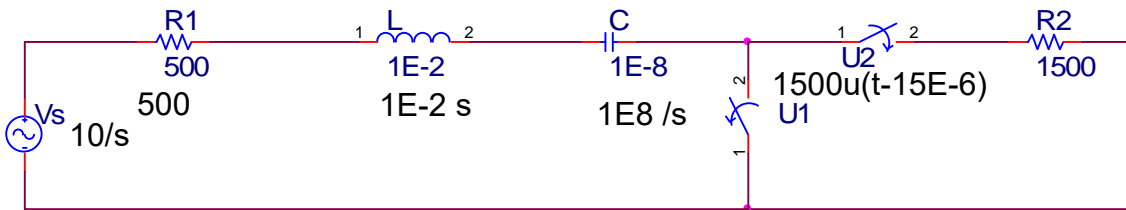

In the above circuit, the source turns on at $t=0$ with a voltage of 10V. Additionally, switch U1 is closed and switch U2 is open. At $15E-6$ s switch U1 opens and switch U2 closes. The source also turns off at $15E-6$ s.

4.1: Use Laplace analysis to determine the voltage across the capacitor as a function of time for $0 < t < 15E-6$ (s)

4.2: Use Laplace analysis to determine the voltage across the capacitor as a function of time for $t > 15E-6$ s

$$\begin{aligned}
 4.1) \quad V_C(s) &= V_s \cdot Z_C / (Z_{R1} + Z_L + Z_C) \\
 V_C(s) &= V_s \cdot 1/(sC) / (R1 + sL + 1/(sC)) \\
 V_C(s) &= V_s \cdot 1/(CL) / (sR1/L + s^2 + 1/LC) \\
 V_C(s) &= 10/s \cdot 1/(1E8 \cdot 1E-2) / (s^2 + s \cdot (500/1E-2) + 1/(1E8 \cdot 1E-2)) \\
 V_C(s) &= 10/s \cdot 1E-6 / (s^2 + s5E4 + 1E-6)
 \end{aligned}$$

$$\begin{aligned}
 V_C(s) &= 1E-5 / s(s^2 + s5E4 + 1E10) \\
 V_C(s) &= 1E-5 / s(s + 25E3 + 96824j)(s + 25E3 - 96824j) \\
 V_C(s) &= A0/s + A1/(s + 25E3 + 96824j) + A1^*/(s + 25E3 - 96824j) \\
 A0 &= 1E-5 / ((s + 25E3 + 96824j)(s + 25E3 - 96824j))|_{s=0} = 0 \\
 A0 &= 1E-5 / (25E3 + 96824j)(25E3 - 96824j) \\
 A0 &= 1E-5 / 1E10 = 1E-15 \\
 A1 &= 1E-5 / s(s + 25E3 - 96824j)|_{s=p1} = -25E3 - 96824j \\
 A1 &= 1E-5 / (-25E3 - 96824j)(-96824j - 96824j) \\
 A1 &= -5.333E-16 + 4.84E8
 \end{aligned}$$

$$\begin{aligned}
 4.2) \quad V_C(s) &= V_s \cdot Z_C / (Z_{R1} + Z_L + Z_C + Z_{R2}) \\
 V_C(s) &= V_s \cdot 1/(sC) / (R1 + sL + 1/(sC) + R2) \\
 V_C(s) &= V_s \cdot 1/(CL) / (sR1/L + s^2 + 1/LC + R2s/L) \\
 V_C(s) &= V_s \cdot 1/(CL) / (s^2 + s(R1 + R2)/L + 1/LC) \\
 V_C(s) &= 10/s \cdot 1/(1E8 \cdot 1E-2) / (s^2 + s \cdot (2000/1E-2) + 1/(1E8 \cdot 1E-2)) \\
 V_C(s) &= 10/s \cdot 1E-6 / (s^2 + s \cdot (2E5) + 1/(1E6))
 \end{aligned}$$