

(1)

ITE - Homework 5Problem 1 BJT V_t , α , β , V_{th}

(a) V_t = thermal voltage = constant =
 $= \frac{kT}{e} = 26 \text{ mV}$ (at 300K)

$\alpha = \frac{I_c}{I_E}$ = Ratio of I_c to I_E =
 = Fraction of I_E that reaches the C
 (C = collector)

Typical values $\alpha \approx 0.95 \dots 0.99$

$\beta = \frac{\alpha}{1-\alpha}$ = Ratio of I_c to I_B

β derives itself from α

Typical values $\beta \approx 40 \dots 200$

V_{th} = BE diode threshold voltage
 $= 0.7 \text{ V}$ for Si BJTs

(b) α is best suited to understand BJT ②
 α = Fraction of E current that reaches C
 α is very close to 1.0

(c) β is relevant in practice

$$\beta = \frac{I_C}{I_B}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

β relates output (current I_C) to input (current I_B). This is of interest to us.


(d) α depends strongly on the base width W_B

$$W_B \downarrow \Rightarrow \alpha \uparrow$$


Note that β also depends on W_B because β depends on α .

Problem 2 BJT characteristics

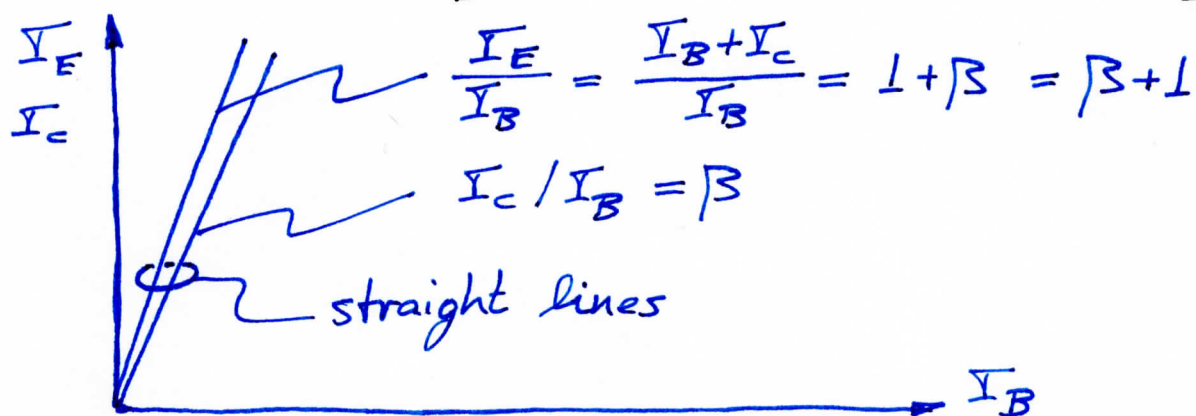
(a) I_E - versus - I_B and I_C - versus - I_B



(b) I_C - versus - V_{BE}

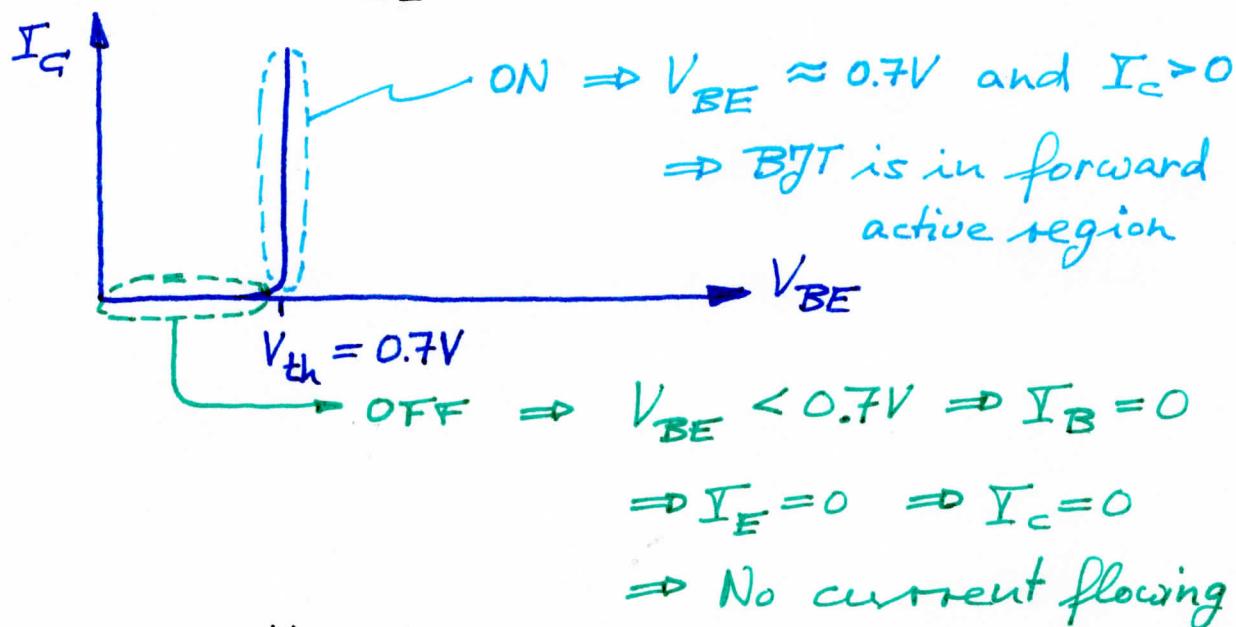

(c) I_C - versus - V_{CE}

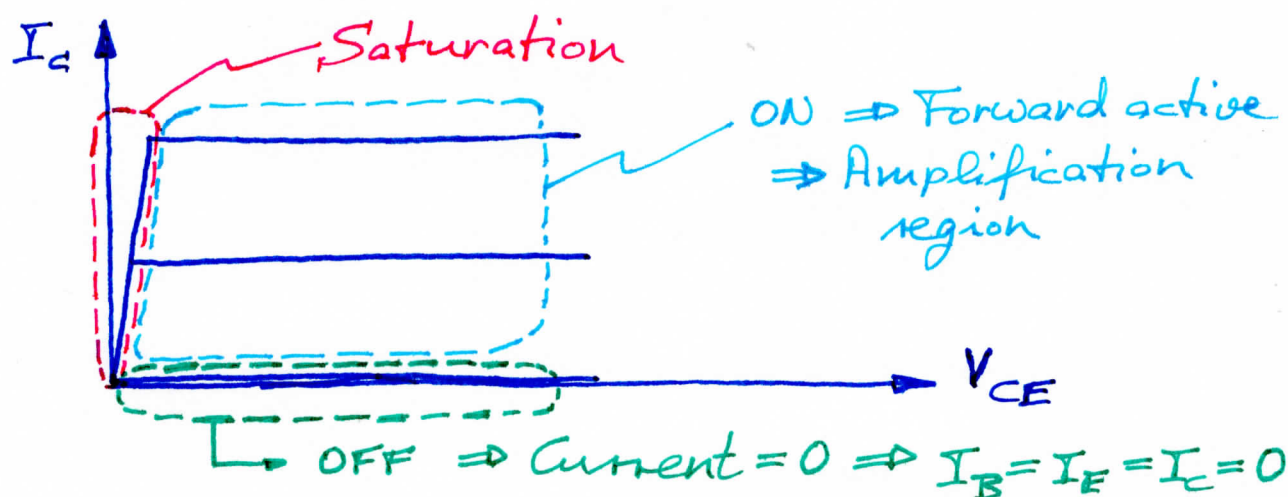





Typical value for $V_{CE, \text{sat}} \approx 0.2V$

Problem 3 BJT circuit


(a) Common-B BJT amplifier

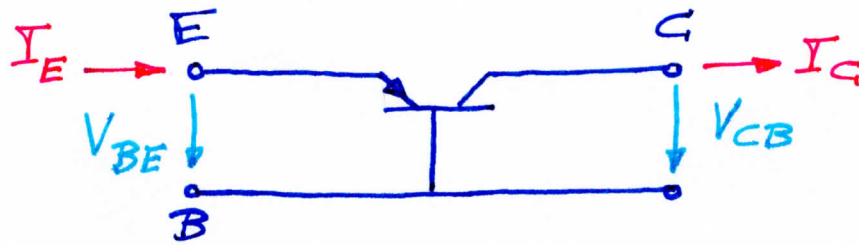

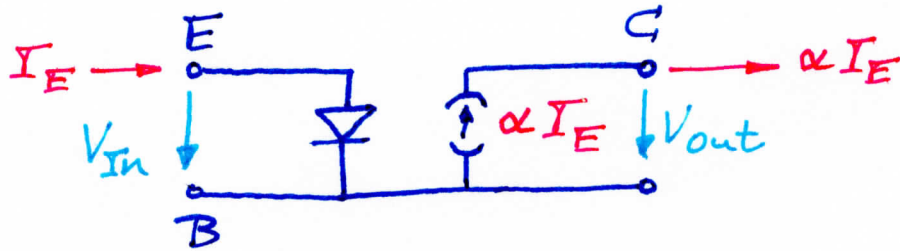(b) Large-signal equivalent circuit
 \Rightarrow BE diode is a diode



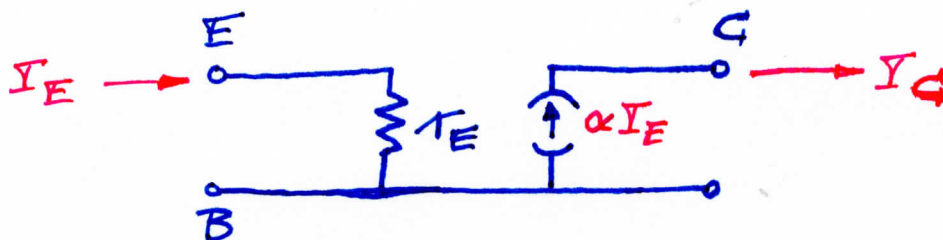(c) Small-signal equivalent circuit
 \Rightarrow BE diode is linearized \Rightarrow Becomes resistor



$r_E = \frac{V_t}{I_E} \Rightarrow r_E$ is small because
 BE diode is forward
 biased

- (d) We prefer a large input resistance (so as to not overload the signal source). The common-B amplifier for this reason is rarely used.