

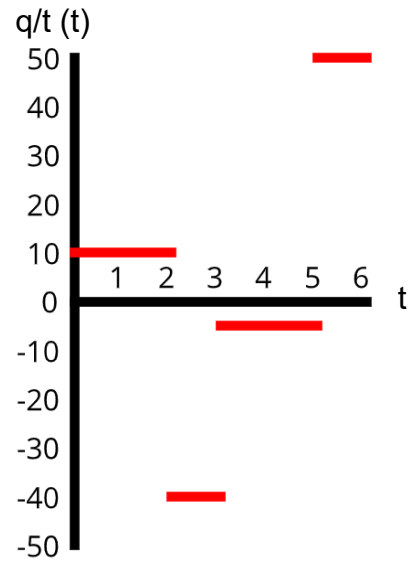


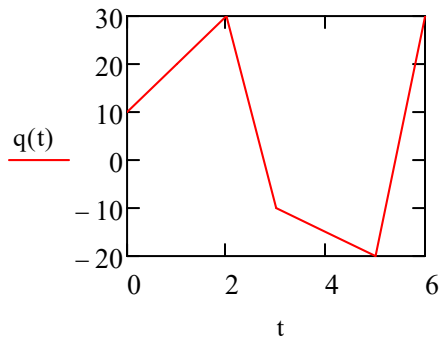1) General Current, Voltage, or Power

The plot below is the net positive charge flowing in a wire vs. time. Sketch the corresponding current during the same period of time.



2) Source devices and Total Power

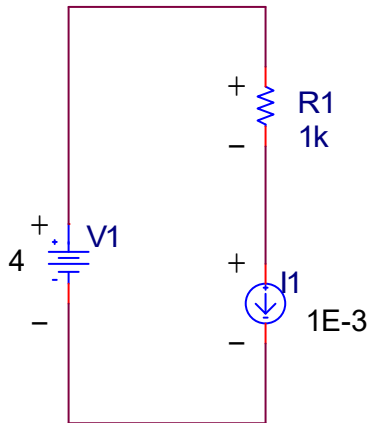

2.1: Determine the current through the voltage source, V1. Include the direction in your answer.

-1mA
(up)

2.2: Determine the voltage across the current source, I1. Include the polarity in our answer

$V=IR$
 $V(R1)=1\text{mA} \cdot 1\text{kohm}=1\text{V}$
 $(4-1)-0=3$
 $+3\text{V}$
 (positive up)

2.3: Determine the power supplied/consumed by each component and show they balance to 0W.


V1:
 $P=IV$
 $P=-1\text{mA} \cdot 4\text{V}=-4\text{mW}$ (4mW supplied)

I1:
 $P=1\text{mA} \cdot 3\text{V}=3\text{mW}$ (3mW consumed)

R1:
 $P=1\text{mA} \cdot 1\text{V}=1\text{mW}$ (3mW consumed)

$-4\text{mW}+3\text{mW}+1\text{mW}=0\text{mW}$

3) Nodal voltages/voltage drops/currents

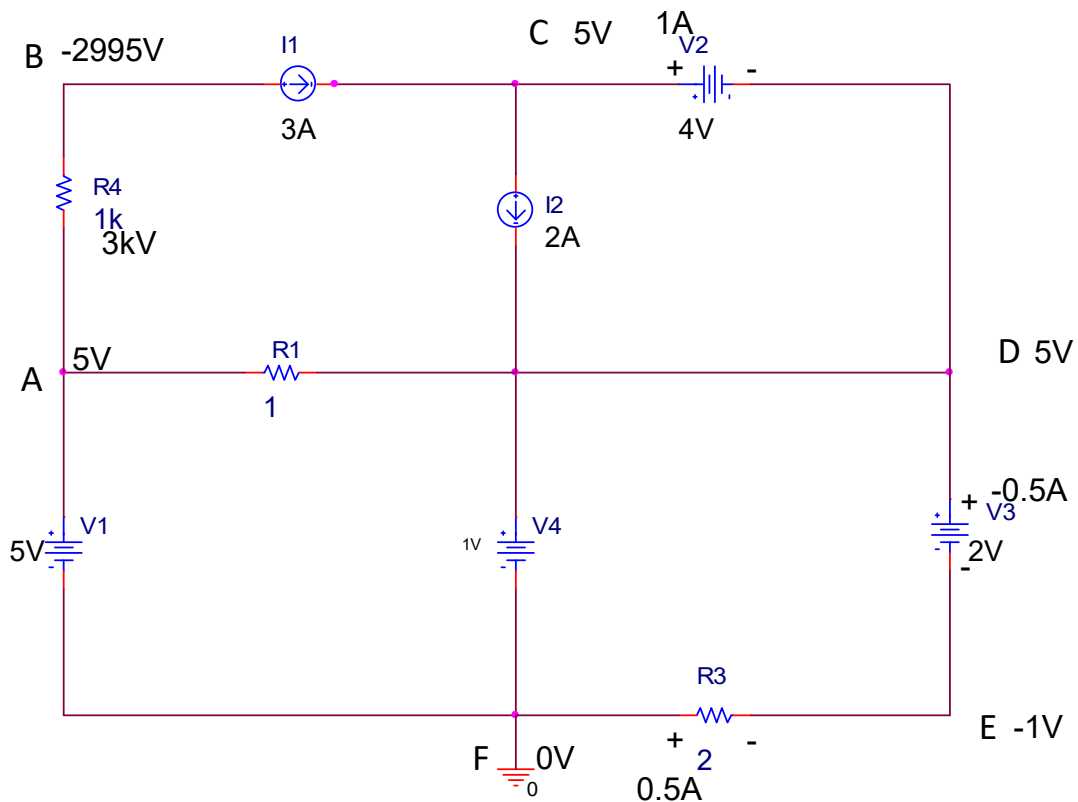

3.1: How many nodes are in the above circuit?

3

3.2: Determine the voltage at every node.

A: 5V B: -2995V C: 5V D: 1V E: -1V F: 0V

3.3: Determine the current through R_3 , V_2 , and V_3 (label or indicate current direction for full credit)

R_3 : 0.5A V_2 : 1A V_3 : -0.5A


4) KVL/KCL

In this circuit,

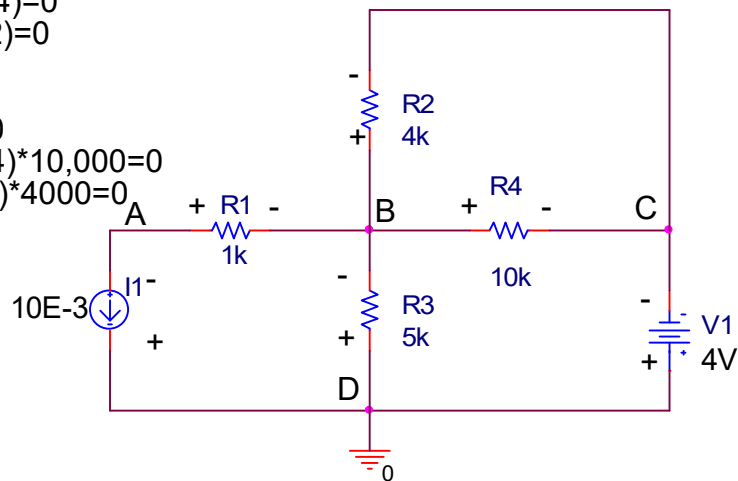4.1: Determine four linearly independent equations for the voltage across the resistors. You will have to use a combination of Ohm's law, KCL, and KVL.

Redraw the circuit with polarities for full credit.

$$\begin{aligned} \text{A: } -I(I_1) + I(R_1) &= 0 \\ \text{B: } -I(R_1) + I(R_2) - I(R_3) + I(R_4) &= 0 \\ \text{V1R3R4: } -V(V_1) + V(R_3) + V(R_4) &= 0 \\ \text{R3V1R2: } -V(R_3) + V(V_1) - V(R_2) &= 0 \\ V=IR \quad I=V/R \\ \text{A: } .01 + I(R_1) &= 0 \\ \text{B: } -I(R_1) + I(R_2) - I(R_3) + I(R_4) &= 0 \\ \text{V1R3R4: } -4 + I(R_3) * 5000 + I(R_4) * 10,000 &= 0 \\ \text{R3V1R2: } -I(R_3) * 5000 + 4 - I(R_2) * 4000 &= 0 \end{aligned}$$




4.2: Set up these equations in matrix/vector form.

$$\begin{bmatrix} I() & R1 & R2 & R3 & R4 & RHS \\ 1 & 0 & 0 & 0 & 0 & -0.01 \\ -1 & 1 & -1 & 1 & 0 & 0 \\ 0 & 0 & 5000 & 10000 & 4 & 0 \\ 0 & -4000 & -5000 & 0 & -4 & 0 \end{bmatrix}$$

4.3: Solve for the voltages across each resistor.

	$V=IR$		
$I(R_1) = -0.01$	$V(R_1) = -0.01 * 1000$	$= -10V$	$A = -30.727272V$
$I(R_2) = -0.004181818$	$V(R_2) = -0.004181818 * 4000$	$= -16.727272V$	$B = -20.727272V$
$I(R_3) = 0.0041454545$	$V(R_3) = 0.0041454545 * 5000$	$= 20.727272V$	$C = -4V$
$I(R_4) = -0.0016727272$	$V(R_4) = -0.0016727272 * 10000$	$= -16.727272V$	$D = 0V$

5) KVL/KCL

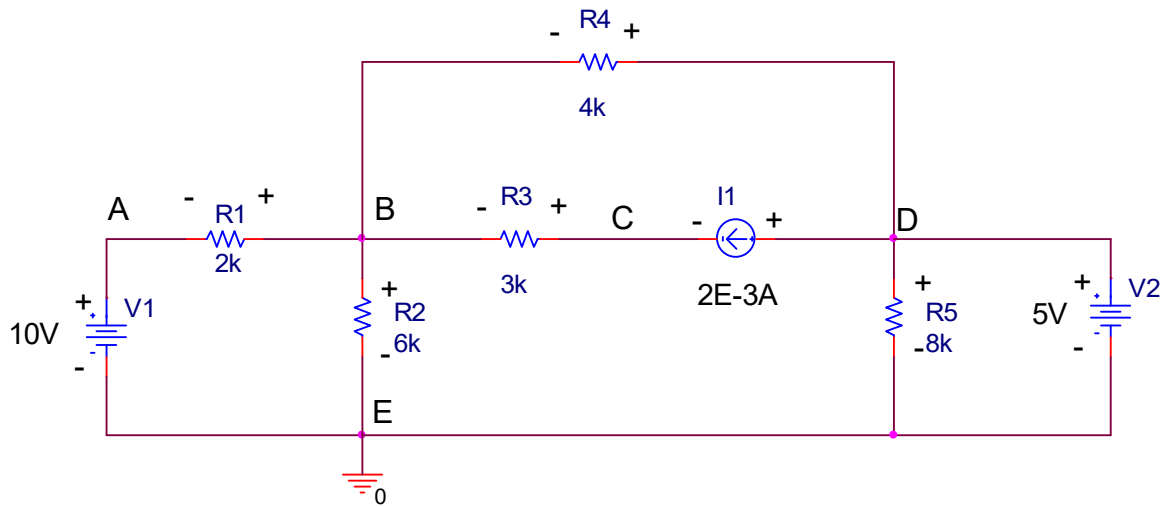

In the above circuit,

5.1: Determine five linearly independent equations for the voltage across the resistors. You will have to use a combination of Ohm's Law, KCL, and KVL.

5.2: Set up these equations in matrix/vector form.

5.3: Solve for the currents through each resistor. Use some software like Maple or Matlab or online tools.

$$B: I(R1) + I(R2) - I(R3) - I(R4) = 0$$

$$C: I(R3) - I(I1) = 0$$

$$V1R1R2: -V(V1) - V(R1) + V(R2) = 0$$

$$V2R5: -V(V2) + V(R5) = 0$$

$$R2R4R5: -V(R2) - V(R4) + V(R5) = 0$$

$$V = IR$$

$$B: I(R1) + I(R2) - I(R3) - I(R4) = 0$$

$$C: I(R3) - .002 = 0$$

$$V1R1R2: -10 - I(R1) \cdot 2000 + I(R2) \cdot 6000 = 0$$

$$V2R5: -5 + I(R5) \cdot 8000 = 0$$

$$R2R4R5: -I(R2) \cdot 6000 - I(R4) \cdot 4000 + I(R5) \cdot 8000 = 0$$

I()	R1	R2	R3	R4	R5	RHS
1	1	1	-1	-1	0	0
0	0	0	1	0	0	.002
-2000	6000	0	0	0	0	10
0	0	0	0	0	8000	5
0	-6000	0	-4000	8000	0	0

$$I(R1) = -.0005$$

$$I(R2) = .0015$$

$$I(R3) = .002$$

$$I(R4) = -.001$$

$$I(R5) = .000625$$

$$V = IR$$

$$V(R1) = -.0005 \cdot 2000 = -1V$$

$$V(R2) = .0015 \cdot 6000 = 9V$$

$$V(R3) = .002 \cdot 3000 = 6V$$

$$V(R4) = -.001 \cdot 4000 = -4V$$

$$V(R5) = .000625 \cdot 8000 = 5V$$

$$A = 10V$$

$$B = 9V$$

$$C = 15V$$

$$D = 5V$$

$$E = 0V$$

$$t := 0, 1 \dots 6$$

$$q(t) := \text{if}(t \leq 2, 10 + 10 \cdot t, \text{if}(t \leq 3, -5t + 5, \text{if}(t \leq 4, -5t + 5, \text{if}(t \leq 5, -5t + 5, \text{if}(t \leq 6, 5t, 0))))))$$