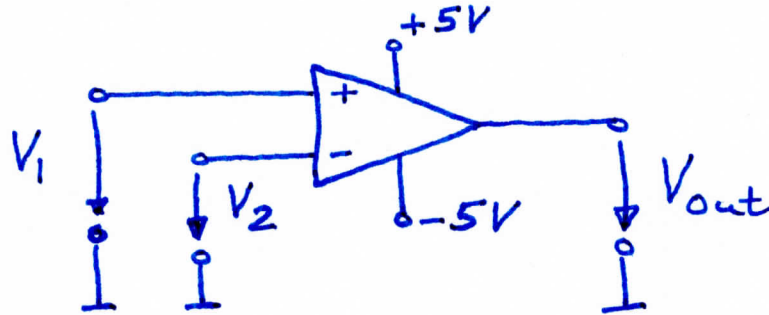


# ITE - Homework 02 - Solution

①

Problem 01 Op Amp  $V_{CC} = +5V$   $-V_{CC} = -5V$

(a) Op Amp circuit without feedback



Explain function :


$$\text{If } V_1 > V_2 \Rightarrow V_{out} = +5V$$

$$\text{If } V_1 < V_2 \Rightarrow V_{out} = -5V$$

$$\text{If } V_1 = V_2 \Rightarrow V_{out} = 0V$$

Name of circuit: Comparator

(b) **LHS** circuit

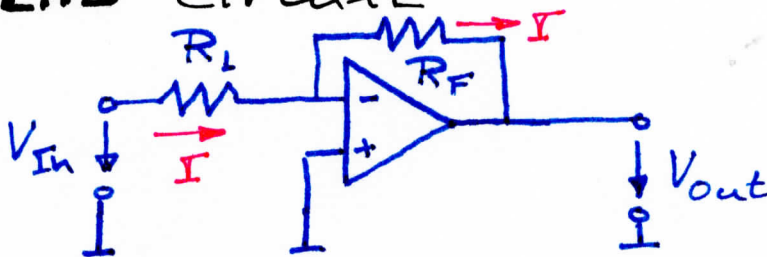


$$\text{KVL: } V_{In} = R_L I$$

$$\text{KVL: } IR_F + V_{out} = 0 \Rightarrow V_{out} = -IR_F$$

$$\Rightarrow A_{voc} = \frac{V_{out}}{V_{In}} = \frac{-IR_F}{IR_L} = -\frac{R_F}{R_L} = -1$$

RHS circuit

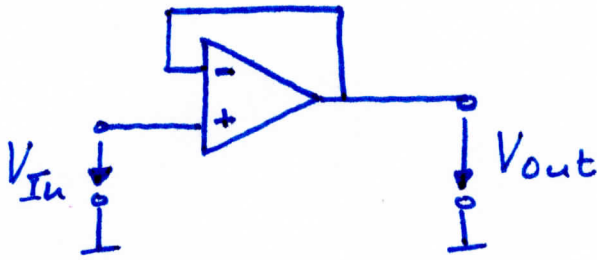

KVL  $V_{In} = V_{out}$

$$\Rightarrow A_{voc} = \frac{V_{out}}{V_{In}} = 1$$

$\Rightarrow$  Circuit may be called "voltage follower".

(c) Common feature: Both feedback elements feed back to the inverting input terminal of the Op Amp.


(d) Feedback goes to non-inverting input!  
 $\Rightarrow$  Runaway circuit  $\Rightarrow$  Not useful.

LHS circuit


$$A_{voc} = \infty$$

RHS circuit

$$A_{voc} = -\infty$$

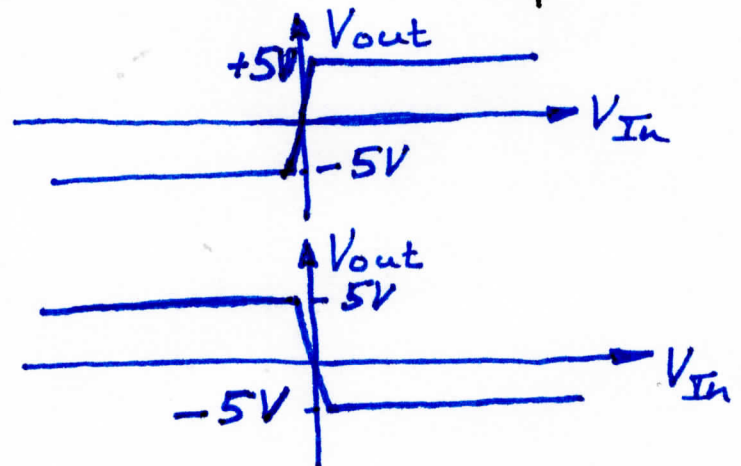

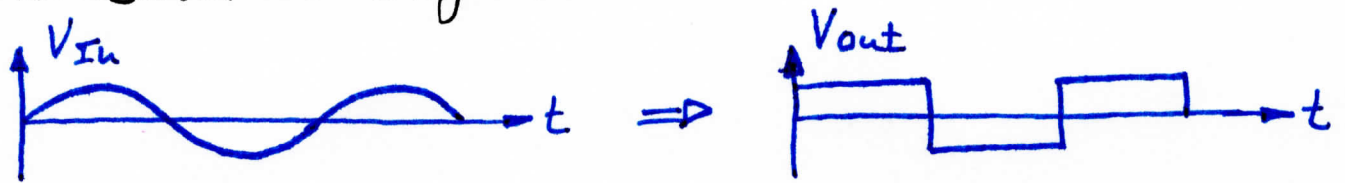(e) Circuits are not useful to amplify sinusoidal signal



$\Rightarrow$  Output signal is strongly distorted.

(f) LHS circuit

$$V_{in} = 1\mu V \Rightarrow V_{out} = +5V$$


$$V_{in} = -1\mu V \Rightarrow V_{out} = -5V$$

(g) RHS circuit

$$V_{in} = 1\mu V \Rightarrow V_{out} = -5V$$

$$V_{in} = -1\mu V \Rightarrow V_{out} = +5V$$


(h) LHS circuit

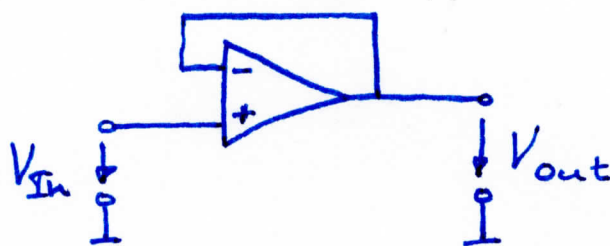

$$KVL: V_{in} = V_{out}$$

$$\Rightarrow A_{voc} = 1$$

RHS circuit

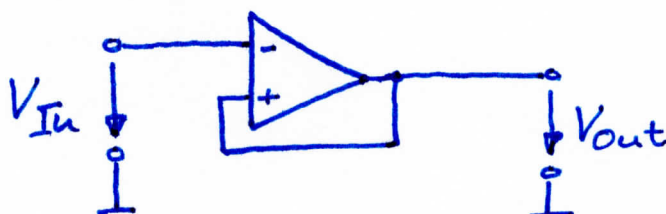

Positive feedback!

$\Rightarrow$  Runaway configuration

$$\Rightarrow A_{voc} = -\infty$$

④

The LHS circuit is a "voltage follower" because  $V_{out}$  follows  $V_{in}$ , that is,  $V_{out} = V_{in}$ .

## Problem 2

(a) Superposition Theorem: The output voltage is the sum of the two output voltages caused by  $V_1$  and  $V_2$ .

The theorem can be used for linear amplifiers. An Op Amp is a linear amplifier. Therefore the conditions are met.

(b) Employment of Superposition Theorem

$V_{out}$  due to  $V_1$ :

$$V_2 = 0 \Rightarrow \oplus \text{ at GND}$$

$$\text{KVL} \quad V_1 = IR_1$$

$$\text{KVL} \quad V_{out} = -IR_F$$

Eliminating  $I$  from the two eqns. yields

$$V_{out} = -\frac{R_F}{R_1} V_1$$

$V_{out}$  due to  $V_2$ :

$$V_1 = 0$$

$$V_{\oplus} = V_2 \frac{R_G}{R_2 + R_G}$$

(Voltage divider)

$$V_{\ominus} = V_{out} \frac{R_1}{R_F + R_1}$$

(Voltage divider)

$$V_{\oplus} = V_{\ominus} \Rightarrow V_{out} \frac{R_1}{R_F + R_1} = V_2 \frac{R_G}{R_2 + R_G} \quad (6)$$

$$\Rightarrow V_{out} = V_2 \frac{R_G}{R_2 + R_G} \frac{R_F + R_1}{R_1}$$

Superposition

$$V_{out} = -\frac{R_F}{R_1} V_1 + \frac{R_G}{R_2 + R_G} \frac{R_F + R_1}{R_1} V_2$$

↳ Superposition

$$(c) \quad R_1 = R_F = R_2 = 1 \text{ k}\Omega \quad R_G = 100 \Omega$$

$$\Rightarrow V_{out} = -V_1 + \frac{100 \Omega}{1 \text{ k}\Omega + 100 \Omega} \times 2 \times V_2$$


$$= -V_1 + \frac{2}{11} V_2$$


---




# Problem 3

(a) Black box

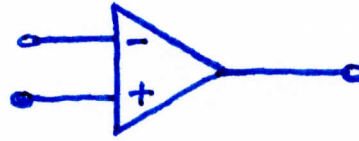

Equivalent circuit

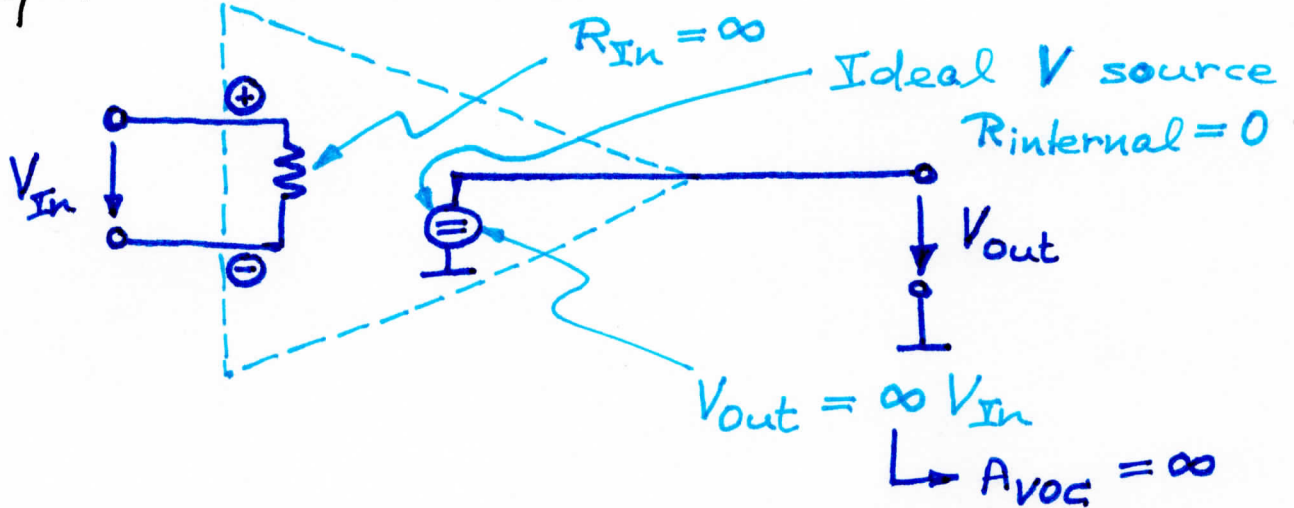

(b)  $R_{in} = \infty$

Input resistance

$A_{voc} = \infty$

OC voltage amplification

$R_{out} = 0$

Output resistance

↳ Internal resistance of ideal V source

## Problem 4

(a) Op Amp 1 is an ideal Op Amp. Accordingly, the voltage at its output is only determined by the ideal output voltage source of Op Amp 1. This voltage will not change for any voltage  $V_2$  or  $V_3$ .

(b) Stage 1 = Inverting amplifier

$$A_{voc} = \frac{V_{OpAmp1}}{V_{In}} = - \frac{R_F}{R_1}$$

$$\Rightarrow V_{OpAmp1} = - \underbrace{\frac{R_F}{R_1}}_{\substack{\rightarrow R_F = R_1 \Rightarrow \text{same } R}} V_{In} = -V_{In}$$

Stage 2

$$V_- = \underbrace{V_{OpAmp1} \frac{R_2}{R_3 + R_2}}_{\rightarrow \text{Voltage divider}} = \frac{1}{2} V_{OpAmp1}$$

$$V_+ = 1V$$

Stage 2 has no feedback  $\Rightarrow$  Comparator



⑨

$$\text{If } V_- > 1V \Rightarrow V_{out} = -5V$$

$\hookrightarrow \text{Op Amp 2}$

$$\text{If } V_- < 1V \Rightarrow V_{out} = +5V$$


$$\text{Recall } V_- = \frac{1}{2} V_{OpAmp1} = -\frac{1}{2} V_{In}$$

Therefore

$$\text{If } V_{In} < -2V \Rightarrow V_- > 1V \Rightarrow V_{out} = -5V$$

$$\text{If } V_{In} > -2V \Rightarrow V_- < 1V \Rightarrow V_{out} = +5V$$

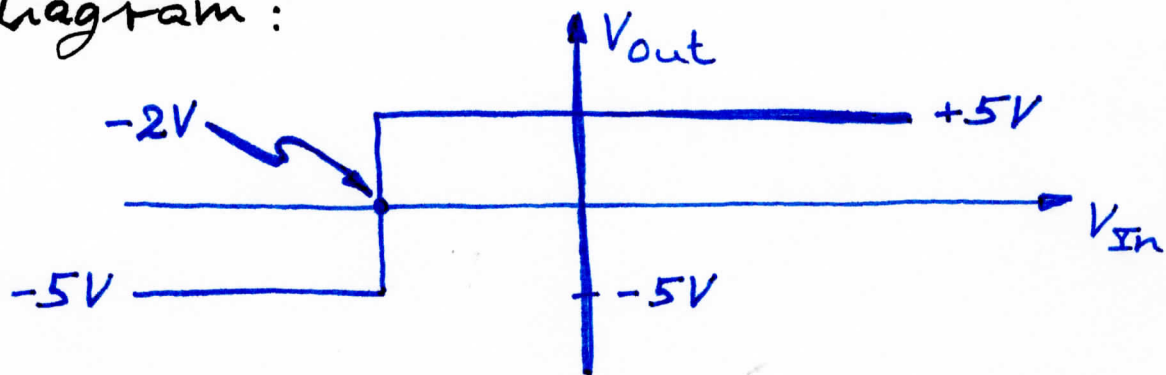We can express this in terms of a diagram:



## Problem 5

(a) True.

The two terms are frequently used synonymously.

(b) True.

An ideal Op Amp has zero output resistance (zero internal resistance of the voltage source).