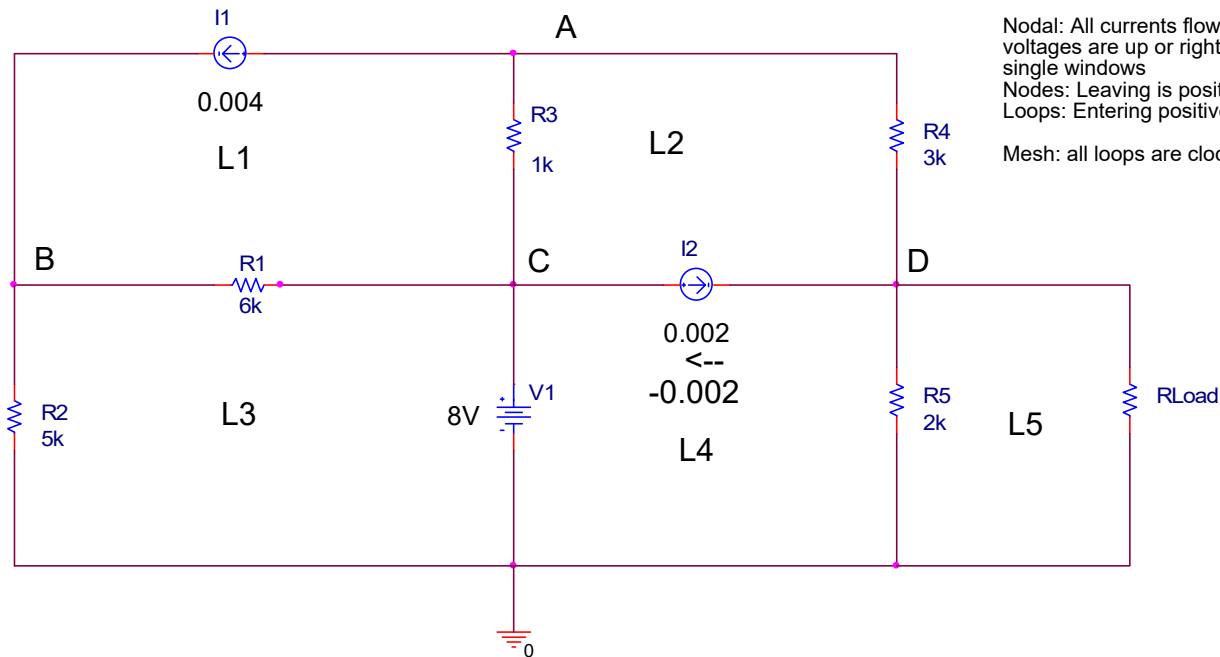


2) Thevenin/Norton Voltage



Nodal: All currents flow down or left, all positive voltages are up or right, all loops are clockwise single windows
 Nodes: Leaving is positive, entering is negative.
 Loops: Entering positive is positive
 Mesh: all loops are clockwise

On the above circuit, using any method, find the a) thevenin voltage, b) thevenin resistance, and c) norton current. Draw the schematics of the norton and thevenin circuits for full credit. Confirm your values by any method.

a) voltage

$$\begin{aligned} \text{A: } & .004 + I(R3) + I(R4) = 0 \\ \text{B: } & -.004 - I(R1) + I(R2) = 0 \\ \text{D: } & -.002 - I(R4) + I(R5) = 0 \\ \text{L3: } & 8 - 5000 \cdot I(R2) - 6000 \cdot I(R1) = 0 \\ \text{L24: } & -8 - 1000 \cdot I(R3) + 3000 \cdot I(R4) + 2000 \cdot I(R5) = 0 \end{aligned}$$

$$\begin{aligned} \text{R1: } & -1.0909\text{mA} \quad -6.5454\text{V} \\ \text{R2: } & 2.9090\text{mA} \quad 14.5454\text{V} \\ \text{R3: } & -4.0000\text{mA} \quad -4.0000\text{V} \\ \text{R4: } & 0.0000\text{mA} \quad 0.0000\text{V} \\ \text{R5: } & 2.0000\text{mA} \quad 4.0000\text{V} \end{aligned}$$

$$V_{th} = 4\text{V}$$

b) resistance

$$V_{test} = 1\text{V}, \text{ circuit simplifies, } R_{th} = 1.333\text{k ohm}$$

c) current

$$V_{th} = I_{no} \cdot R_{th}, \quad 4 = I_{no} \cdot (4/3)\text{k},$$

$$I_{no} = 3\text{mA}$$

confirm) test $R_{Load} = 1\text{k}$

$$\begin{aligned} \text{A: } & .004 + I(R3) + I(R4) = 0 \\ \text{B: } & -.004 - I(R1) + I(R2) = 0 \\ \text{D: } & -.002 - I(R4) + I(R5) + I(RL) = 0 \\ \text{L3: } & 8 - 5000 \cdot I(R2) - 6000 \cdot I(R1) = 0 \\ \text{L24: } & -8 - 1000 \cdot I(R3) + 3000 \cdot I(R4) + 2000 \cdot I(R5) = 0 \\ \text{L5: } & -2000 \cdot I(R5) + 1000 \cdot I(RL) = 0 \end{aligned}$$

Linsolve, not writing it all down
 $R_L: I = 1.714\text{mA} \quad V = 1.714\text{V}$

$$I = V/R = 4 / ((4/3) + 1)\text{k} = 1.714\text{mA} \quad \checkmark$$

4) Amplifier Circuits



1

5) Amplifier Circuits - Designing problem

a) Design a two stage amplifier such that the output of the first stage is $V_1 = 5 \cdot V_{in}$ and the output of the second stage is $V_2 = -V_1$.

