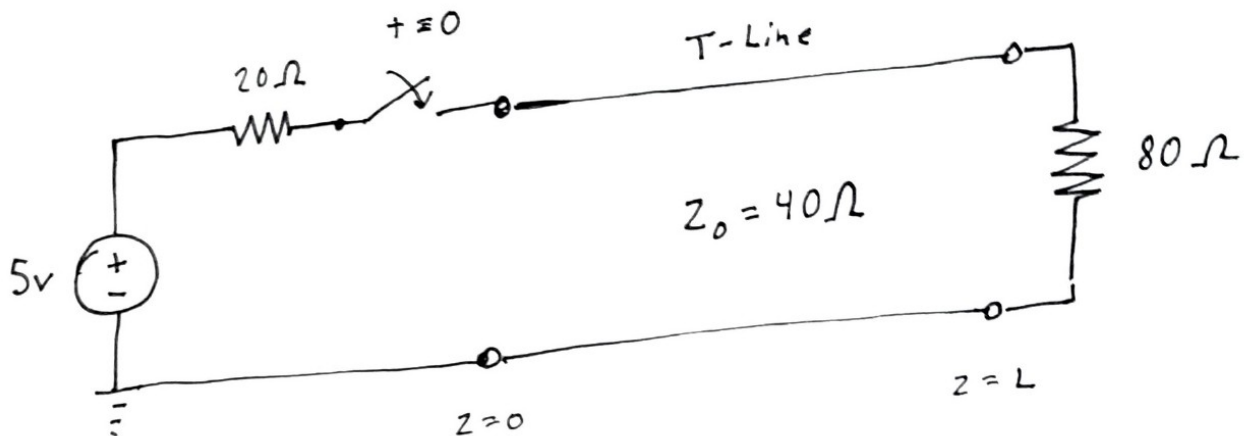


Exam 1 Practice Problems

(optional; not for submission)

1.) Transient Analysis



Consider the circuit above. The voltage source pictured is a DC source. At $t=0$, the switch closes. The transmission line pictured has a propagation velocity of $\frac{1}{2}$ the speed of light and is 300m long.

- What is the amplitude of the initial forward-traveling voltage wave?
- How much time elapses between the closing of the switch and the arrival of the forward-traveling voltage wave at the load?
- Create a bounce diagram for this circuit, showing the amplitude of each voltage and the voltage at both the transmission line input and the load with respect to time t . The bounce diagram should include the first three reflections.
- Graph the voltage at the input of the transmission line with respect to t from the time the switch closes until the time that the third reflection has occurred.


2.) Input Impedance, Reflection and Power

A sinusoidal signal with amplitude 1V and frequency 1 MHz enters an RG-58 transmission line with $Z_0=50\Omega$ and velocity factor 0.6. You place a voltage probe at the load and measure an amplitude of 750mV. The line length is 300m. Approximate the line as having no losses.

- a.) What is the reflection coefficient at the load? What is load impedance?
- b.) What is the wavelength of the signal on the line?
- c.) What is the input impedance for this transmission line and signal once the line reaches steady state?
- d.) Supposed that the line length is increased by 270m. Without doing any calculations, will the input impedance change? Why or why not?
- e.) What is the average power transmitted to the load? What would the average power transmitted to the load be if it were replaced with a different load that was matched to the line?

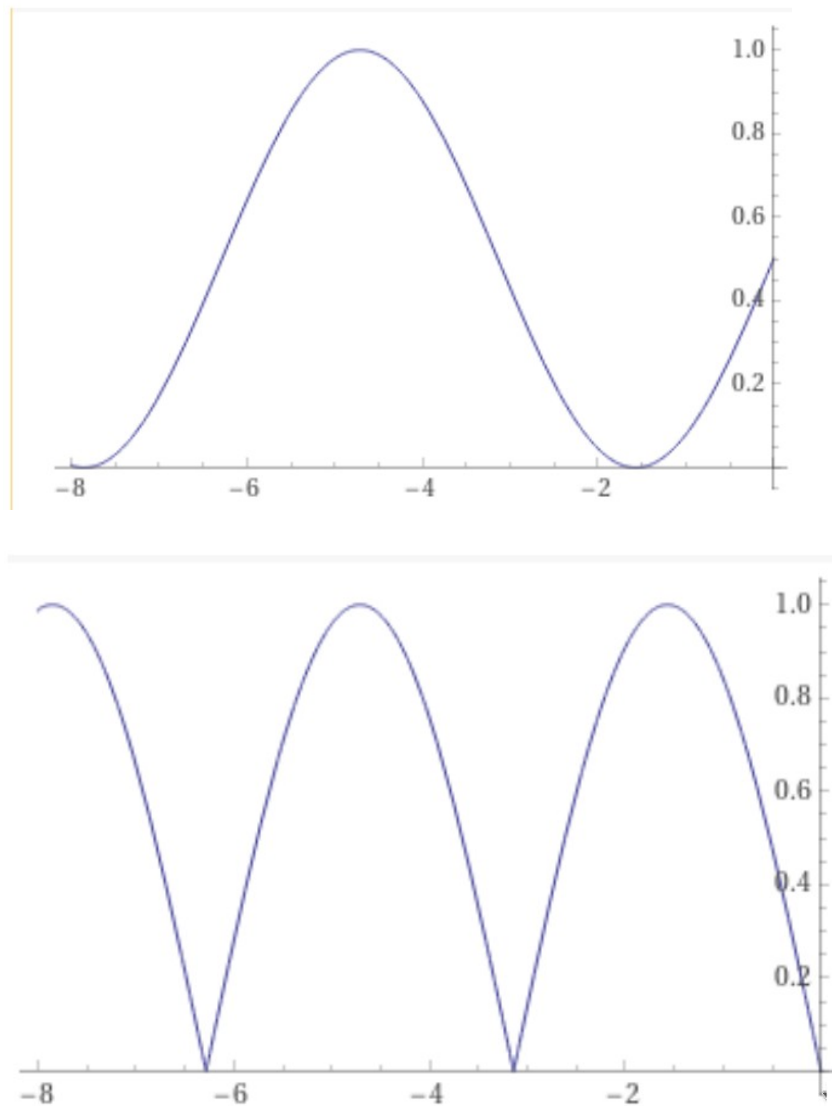3.) Standing Waves

Consider the following 2 voltage plots. Suppose that the rightmost side of the plot represents a load at the end of the transmission line, and moving left on the graph represents moving toward the source. The x-axis units are meters and the y-axis units are volts.




For each of the plots, state the following:

- Could this plot represent a standing wave pattern on a transmission line due to reflection at the load?
- If the answer is yes, assume that the transmission line has $Z_0 = 100\Omega$ and find the standing wave ratio, reflection coefficient, and load impedance.

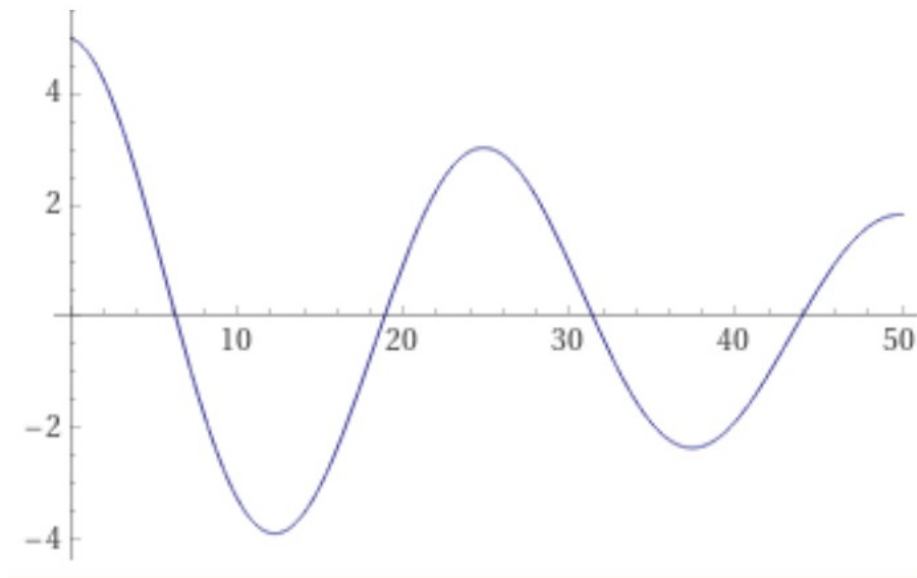4.) Lossy Transmission Line

The following graph represents a voltage propagating on a lossy transmission line. The y axis is measured in volts and the x axis is measured in meters. Note that at $z=0$, the amplitude is 5V and at $z=50$, the amplitude is 2V



What is the attenuation constant? What is the propagation constant?

5.) Low-Loss Transmission Line

Assume that a transmission line has an inductance per length of 100 microhenries per meter and a capacitance per unit length of 100 picofarads per meter. It also has a resistance per unit length of 0.2 ohms per meter.

- Is it reasonable to approximate the line as being low-loss at 1 kHz? (We will state that if the impedance of the series resistance is less than 1% of the impedance of the series inductance, we can use the low-loss approximation.)
- Is it reasonable to approximate the line as being low-loss at 1 MHz?
- You are tasked with adding a resistor in parallel to the line every 10m in order to make the line dispersionless. What value of resistor do you choose?

6.) Online Exercises

[Waves and Phasors](#)

[Transmission Lines](#)