

Homework 11**Due April 26nd****Problems:**

1. Book Problem 9.18: Reminder, a Zener diode's voltage is the reverse-bias voltage. It has a normal forward-bias voltage drop. For this problem, these values are 5.1 V and 0.7 V, respectively.
2. Book Problem 9.36: You may use LTspice to do the analysis of the circuit in order to write your discussion on the circuit operation and to produce the response as requested.
3. Book Problem 10.9: $D(\%)$ refers to the duty cycle of the output: the percentage of the period where the output is *high*.
4. Book Problem 10.14.