

Homework 5**Due March 11th**

Note that for the problems below, we are considering non-ideal DC offsets and not effects due to r_d , r_o , or a . Therefore, you should consider these to be ideal, unless specifically stated otherwise.

Problems:

1. Book Problem 5.4
2. -6050 Only: Book Problem 5.10
3. Book Problem 5.20
4. Book Problem 5.27: This problem presents different contributions for V_{OS} , which are all captured by Equation 5.27. For each part of the question, determine the applicable contributions to V_{OS} ; where some may be neglected.